


Network And Circuits Theory Second Assignment 2019-2020

Kitsios Panagiotis 03116007

28-05-2020

My apologies for using English but the dictation software I am using to write this assignment does not support Greek and at the same time for some reason the program rendering the Latex into a PDF keeps failing with Unicode characters. Also all graphs are generated using graphviz.

1 Exercise One

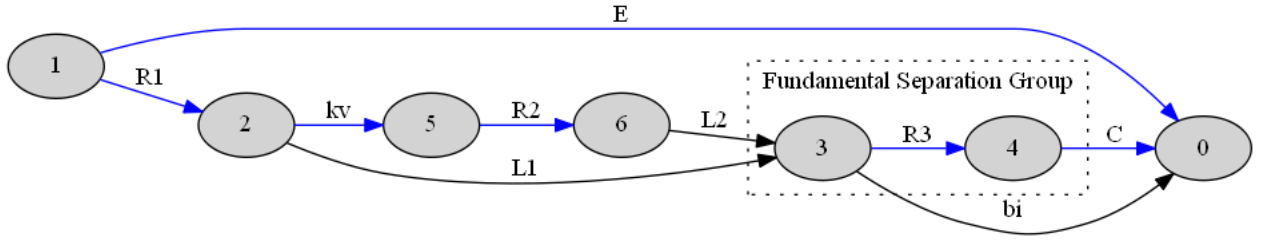

taking into account that

$$i = i_{L2} \quad (1)$$

$$v = E_s - (I_{L1} + I_{L2})R1 \quad (2)$$

From the conservation of current on the fundamental separation group, and from Kirchoffs voltage law across the two fundamental loops we have

$$I_{L1} + I_{L2} = C\dot{V}_C + bI_{L2} \quad (3)$$

$$(E_s - (I_{L1} + I_{L2})R1)(k - 1) + I_{L2}(R3 + R2) + L2\dot{I}_{L2} + V_C = 0 \quad (4)$$

$$(E_s - (I_{L1} + I_{L2})R1) + I_{L1}R3 + L1\dot{I}_{L1} + V_C = 0 \quad (5)$$

Organizing matrix format we get


$$\dot{x}(t) = \begin{pmatrix} 0 & \frac{A}{\frac{1}{C}} & \frac{1-b}{\frac{R1}{L1}} \\ -\frac{1}{L2} & \frac{R1-R3}{\frac{L1}{L2}} & \frac{(k-1)R1-R2-R3}{L2} \end{pmatrix} \begin{pmatrix} V_C(t) \\ I_{L1}(t) \\ I_{L2}(t) \end{pmatrix} + \begin{pmatrix} B \\ 0 \\ -\frac{1}{L2} \end{pmatrix} \begin{pmatrix} u(t) \\ E_s(t) \end{pmatrix}$$

and

$$y(t) = \begin{pmatrix} 0 & C & b \\ 0 & -R1 & -R1 \end{pmatrix} \begin{pmatrix} V_C(t) \\ I_{L1}(t) \\ I_{L2}(t) \end{pmatrix} + \begin{pmatrix} D \\ 0 \\ 1 \end{pmatrix} E$$

2 Exercise Two


The I graph

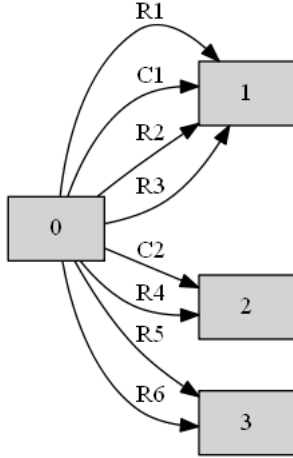

Where

$$\begin{aligned} \boxed{0} &= 0, 1, 3, 5 \\ \boxed{1} &= 2 \\ \boxed{2} &= 4 \\ \boxed{3} &= 6 \end{aligned} \tag{6}$$

and the V graph

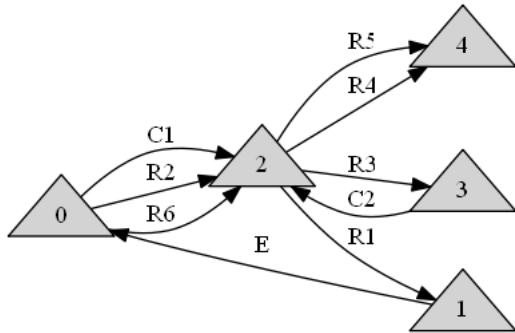

Where the notes correspond to

$$\begin{aligned}
 \triangle &= 0 \\
 \triangle &= 1 \\
 \triangle &= 2, 4, 6 \\
 \triangle &= 3 \\
 \triangle &= 5
 \end{aligned} \tag{7}$$

with the output being


$$V_{out} = E_2 \tag{8}$$

and we arrive at the equations


$$\begin{array}{c} \boxed{1} \\ \boxed{2} \\ \boxed{3} \\ E \end{array} \begin{pmatrix} \triangle & \triangle & \triangle & \triangle \\ R1 + sL1 + R2 & R1 + sL1 & 0 & -sL1 \\ R1 + sL1 - r1 & r2 + R1 + sL1 - r1 + R3 + R4 & -R3 & -sL1 + r1 - R3 \\ r1 & -R3 + r1 & R3 + sL2 & R3 - r1 \\ 1 & 0 & 0 & 0 \end{pmatrix} \begin{pmatrix} E1 \\ E2 \\ E3 \\ E4 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ E \end{pmatrix}$$

3 Exercise Three

The I graph

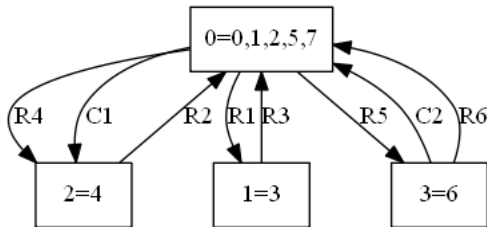

and the V graph

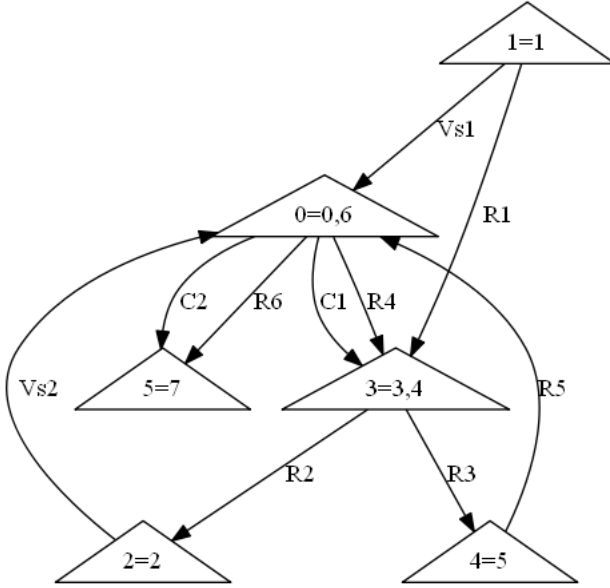

with the output being

$$y = v_{out} = E_5 \quad (9)$$

and we arrive at the equations

$$\begin{array}{c} \boxed{1} \\ \boxed{2} \\ \boxed{3} \\ Vs1 \\ Vs2 \end{array} \begin{array}{c} \triangle \\ \triangle \\ \triangle \\ \triangle \\ \triangle \end{array} \begin{pmatrix} -\frac{1}{R1} & 0 & \frac{1}{R4} + \frac{1}{R3} & -\frac{1}{R3} & 0 \\ 0 & -\frac{1}{R2} & \frac{1}{R4} + sC1 + \frac{1}{R2} & 0 & 0 \\ 0 & 0 & 0 & -\frac{1}{R5} & -sC2 - \frac{1}{R6} \\ 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \end{pmatrix} \begin{pmatrix} E1 \\ E2 \\ E3 \\ E4 \\ E5 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ Vs1 \\ Vs2 \end{pmatrix}$$

As state variables we consider the voltage of the capacitors

$$x = \begin{pmatrix} v_{C1}(t) \\ v_{C2}(t) \end{pmatrix} = \begin{pmatrix} E3 \\ -E5 \end{pmatrix}$$

from those equations it must follow

$$sC1E3 = -(\frac{1}{R4} + \frac{1}{R2})E3 + \frac{Vs2}{R2} \quad (10)$$

and

$$sC2E5 = -\frac{1}{R6}E5 + \frac{R3}{R5}(-\frac{Vs1}{R1} + (\frac{1}{R3} + \frac{1}{R1})E3) \quad (11)$$

So going back to the time domain we obtain


$$\dot{x}(t) = \begin{pmatrix} A & \\ \frac{R3}{R5C2}(\frac{1}{R3} + \frac{1}{R1}) & -\frac{1}{R6C2} \end{pmatrix} \begin{pmatrix} x(t) \\ V_{C2}(t) \end{pmatrix} + \begin{pmatrix} B & \\ \frac{R3}{R5R1C2} & \frac{1}{C1R2} \end{pmatrix} \begin{pmatrix} u(t) \\ V_{s2}(t) \end{pmatrix}$$

and for the output it must hold


$$y(t) = \begin{pmatrix} C & \\ 0 & 1 \end{pmatrix} \begin{pmatrix} x(t) \\ V_{C2}(t) \end{pmatrix} + \begin{pmatrix} D & \\ 0 & 0 \end{pmatrix} \begin{pmatrix} u(t) \\ V_{s2}(t) \end{pmatrix}$$

4 Exercise Four

The I graph

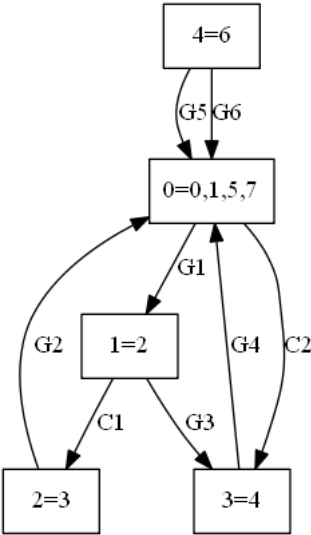

and the V graph

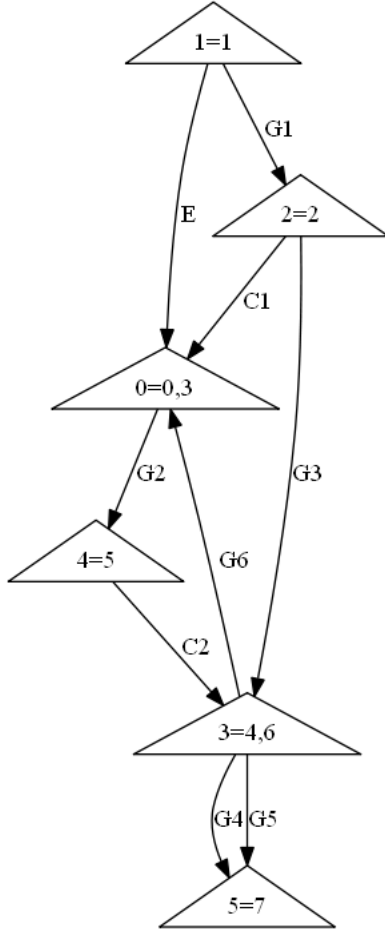

Where the notes correspond to
with the output being

$$V_{out} = E_2 \quad (12)$$

and we arrive at the equations

$$\begin{array}{c} \boxed{1} \\ \boxed{2} \\ \boxed{3} \\ \boxed{4} \\ E \end{array} \begin{array}{cc} \triangle & \triangle \\ \begin{pmatrix} -G1 & G1 + sC1 + G3 \\ 0 & -sC1 \\ 0 & -G3 \\ 0 & 0 \\ 1 & 0 \end{pmatrix} & \begin{array}{cc} \triangle & \triangle \\ \begin{pmatrix} -G3 & 0 \\ 0 & -G2 \\ G3 + sC2 + G4 & -sC2 \\ G5 + G6 & 0 \\ 0 & 0 \end{pmatrix} & \begin{array}{cc} \triangle & \triangle \\ \begin{pmatrix} 0 & 0 \\ 0 & 0 \\ -G4 & -G5 \\ -G5 & 0 \end{pmatrix} \end{array} \end{array} \begin{pmatrix} E1 \\ E2 \\ E3 \\ E4 \\ E5 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ E \end{pmatrix}$$